



Unmasking the J-Pole

Presenting the Di-Pole—a master of disguise

Wesley Cardone, N8QM

June 14, 2022


Presented to the Chelsea Amateur Radio Club

What to Expect to Walk Away With

- If you know nothing of electronics:
 - Expect to leave understanding fundamental concepts
- Maybe you have seen and recognize these things before but have no full grasp of them.
 - Expect to have a much better intuitive feel for how they work.
- Someone having had formal training in basic electronics
 - Expect to leave confident of how these things work.
- Someone who is constantly exposed to electronics and designs.
 - You will have a much more intuitive feel and confidence for how these things work.

What is Presented Tonight

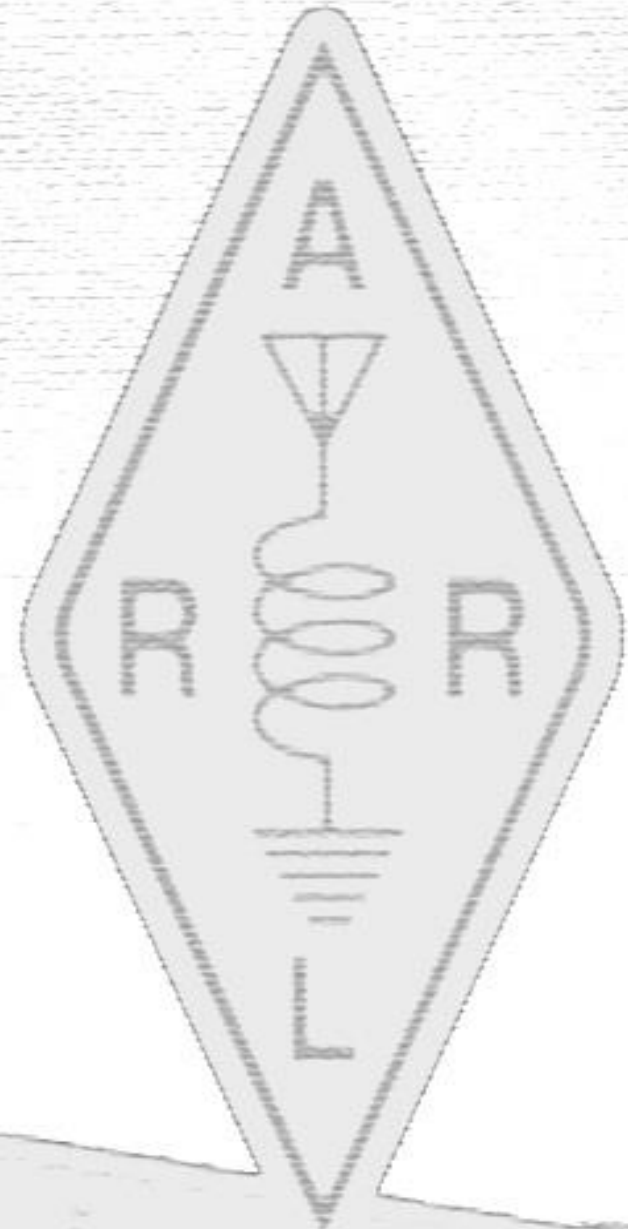- Reactances
 - Capacitive
 - Inductive
- Voltage and Current relationships in
 - electro-magnetics
 - On a di-pole antenna
- The workings of the di-pole antenna
- The workings of the J-Pole antenna



Reactance—What is it?

- Here is what Merriam-Webster says the verb form is.
- “Reactance” is a noun.
 - You tell me what reactance means.
- Does reactance incorporate time?

react verb

 Save Word

re·act | \ rē-'akt  \

reacted; reacting; reacts

Definition of react

intransitive verb

- 1 : to exert a reciprocal or counteracting force or influence —often used with *on* or *upon*
- 2 : to change in response to a stimulus
- 3 : to act in opposition to a force or influence —usually used with *against*
- 4 : to move or tend in a reverse direction
- 5 : to undergo chemical reaction


Understanding Capacitive Reactance

- A capacitor is initially a closed circuit to current.
 - At voltage application it looks like a short.
- When voltage is instantaneously applied,
 - Because the capacitor initially looks like a short...
 - Voltage is zero initially
 - But current freely flows at a maximum but begins to lower toward zero current flow.
 - The capacitor is “reacting” to voltage application.




Capacitive Reactance

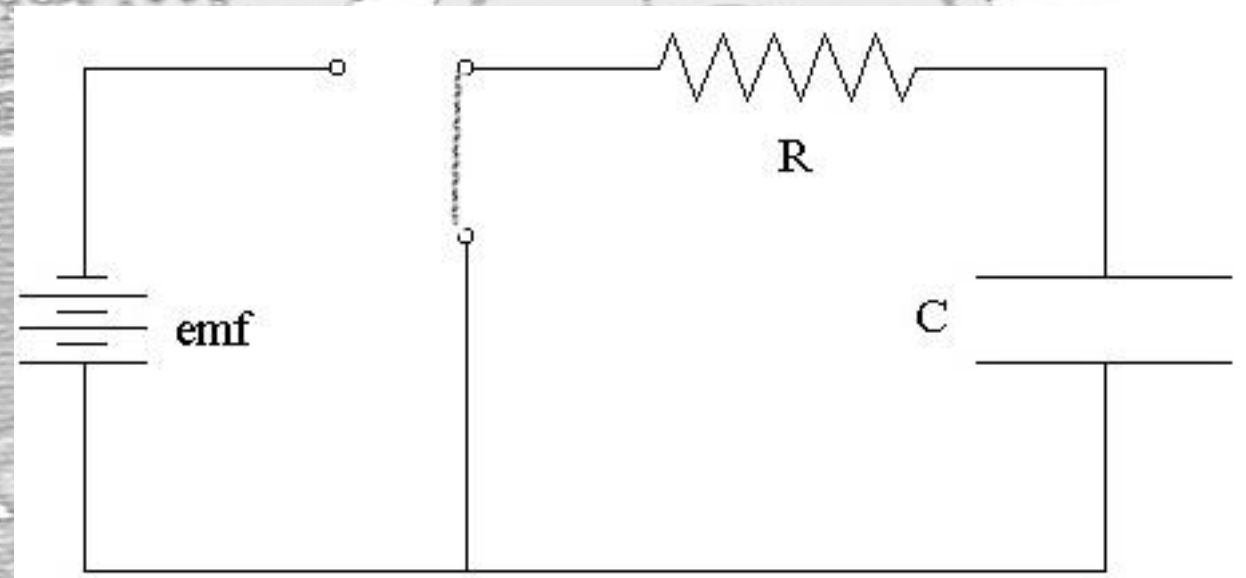- This is an RC (resistance/capacitance) circuit
- EMF source is DC (a battery)
- The switch (SPDT) is initially shorted to ground.
- Shown here, the capacitor has
 - no voltage appearing across it.
 - No current flow.



Capacitive Reactance Transient Response

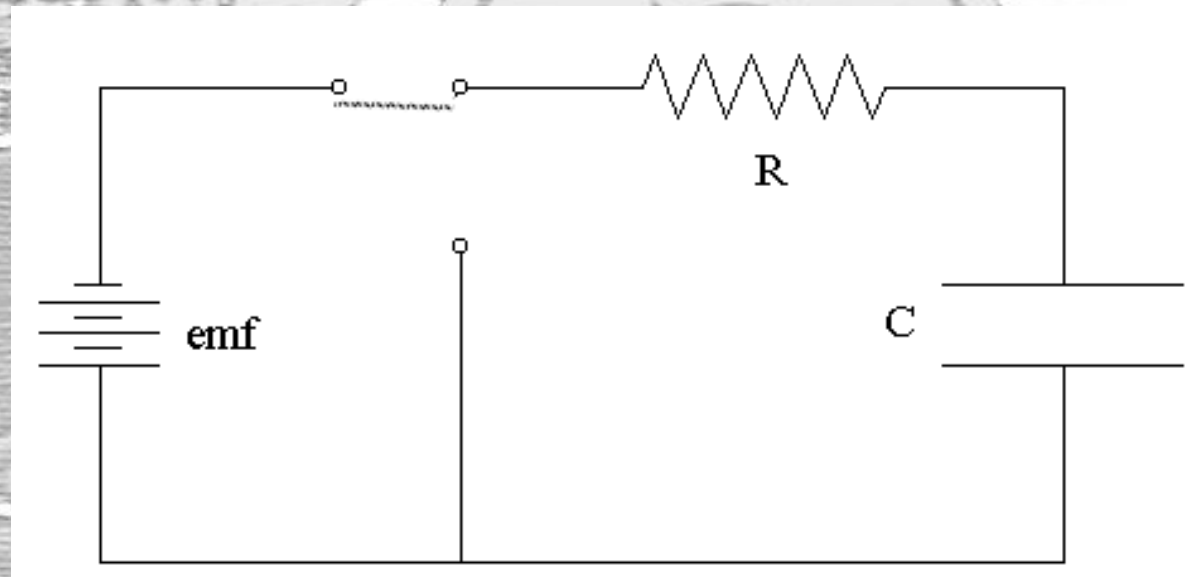- The switch was open but suddenly closed and thereby applies potential to the circuit.
- EMF source is again a battery or DC.
- When the switch closes the capacitor:
 - Still has no voltage appearing across it but, with time, begins to build voltage.
 - The capacitor has maximum current flow but with time, begins to decay toward zero.



What is Phase, anyhow?




- We will be looking at two related signals in the time domain that are...
“out of phase.”

Definition of *phase* (Entry 1 of 2)

- 1** : a particular appearance or state in a regularly recurring cycle of changes
// phases of the moon
- 2 a** : a distinguishable part in a course, development, or cycle
// the early phases of her career
b : an aspect or part (as of a problem) under consideration
- 3** : the point or stage in a period of uniform circular motion, harmonic motion, or the periodic changes of any magnitude varying according to a simple harmonic law to which the rotation, oscillation, or variation has advanced from its standard position or assumed instant of starting
- 4** : a homogeneous, physically distinct, and mechanically separable portion of matter present in a nonhomogeneous physicochemical system
- 5** : an individual or subgroup distinguishably different in appearance or behavior from the norm of the group to which it belongs
also : the distinguishing peculiarity


Phase of Voltage and Current--Capacitive

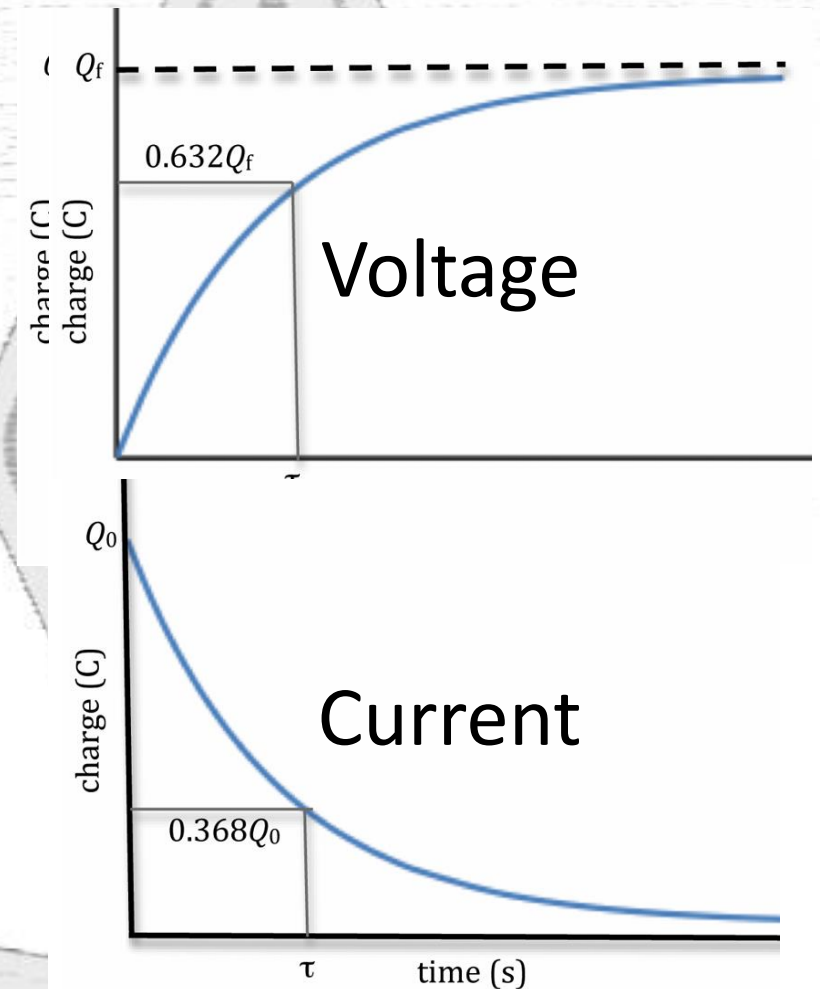- What is the phase relationship in a capacitive circuit of the two signals, voltage and current?
- The answer is NOT intuitive yet:
 - Voltage leads (comes before) the current
 - Current leads (comes before) the voltage
- Think of it this way:
 - We get current first (leads)
 - We get voltage last (lags)




Capacitive in an AC Circuit

- To make phase intuitive we switch from the time domain to the frequency domain.
- DC is now AC so we drop the switch
 - Polarity effectively switching ON and OFF constantly somewhat like a switch.
- Phase relationship now finally becomes intuitive.
 - The current comes first
 - Followed by the voltage
 - Therefore, current LEADS the voltage
- Further, now we can double back to see intuitively in the time domain.

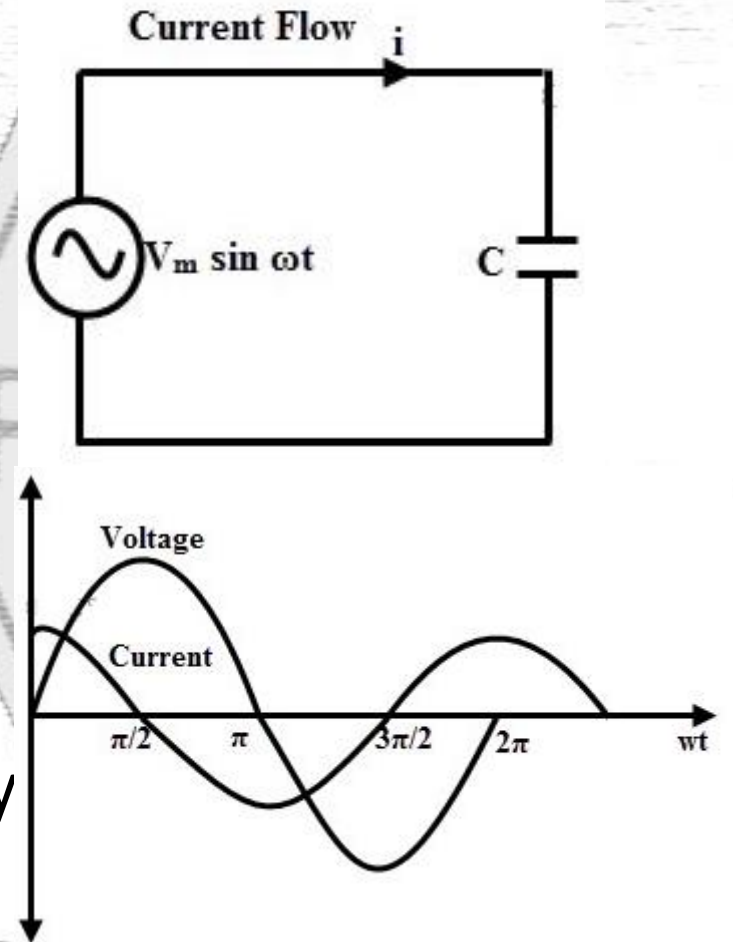



Inductive Reactance

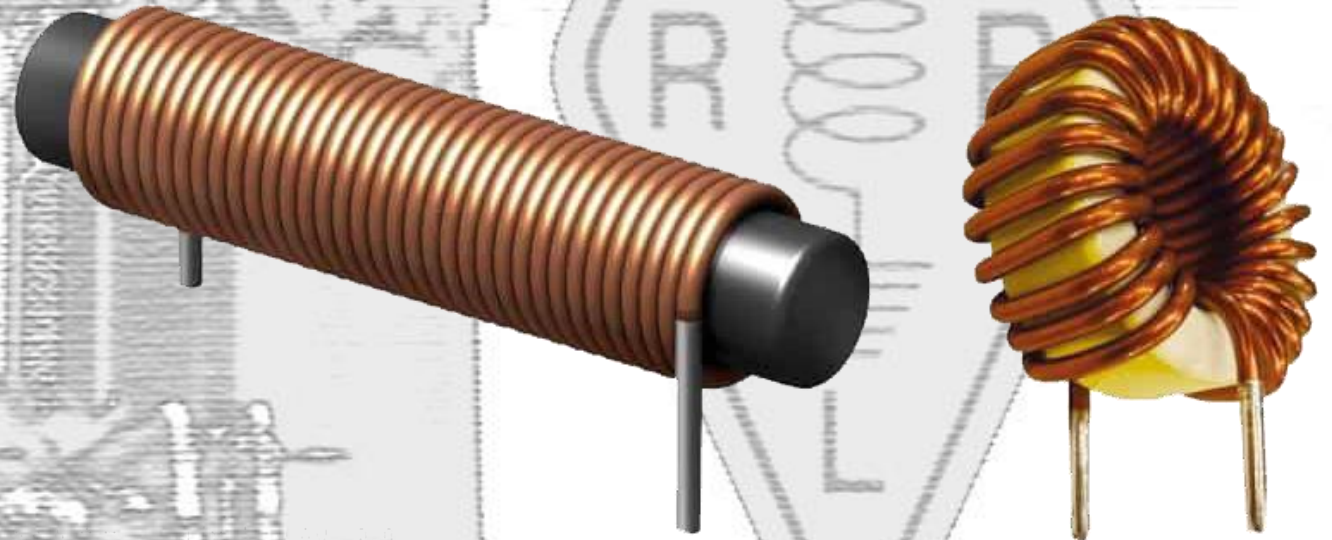- An inductor initially opposes current flow changes.
- At an initial voltage application an inductor looks like an open.
 - If you don't know what an "open" is, it will be shown in a couple of slides.




Inductor in Time Domain

- Start with switch open
 - Any energy drains from circuit to ground.
- Switch closes
 - Places potential across shunt resistor and the series inductor-resistor pair.
 - Inductor refuses to conduct any current initially and therefore drops the full DC potential.
 - Load resistor drops nothing.
- With time...
 - Inductor conducts some current
 - Load resistor shares that same current and drops an Ohm's Law worth of voltage.
- Not intuitive yet: Voltage leads current.

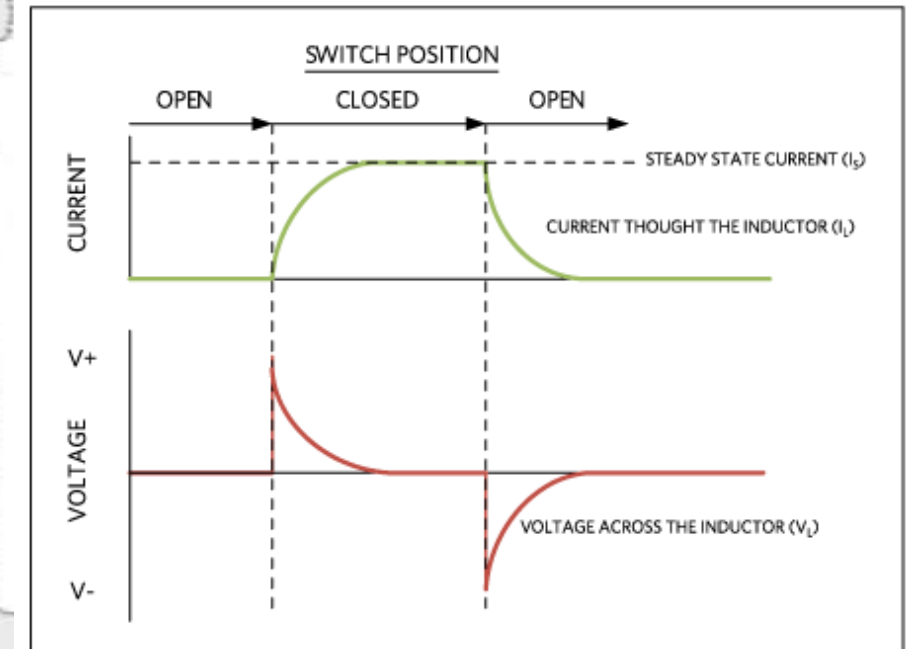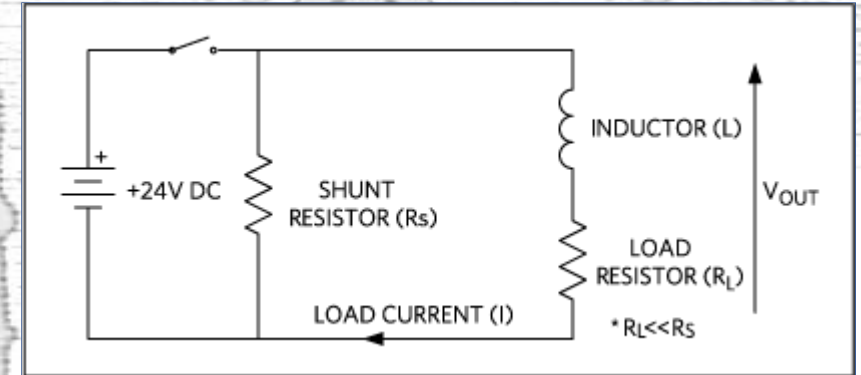


Voltage and Current in Frequency Domain

- What is the phase relationship in an inductive circuit of the voltage with respect to the current?
 - Voltage leads (comes before) the current
 - Current leads (comes before) the voltage
- Why?
 - Potential changes trying to push a current change but the inductor refuses any change at that instant in time.
 - Potential across the inductor rises to satisfy Ohm's Law.
 - Inductor allows some current change with time.
 - Voltage then decreases to continue satisfying Ohm's Law.
- Further, now we can see intuitively in the time domain.

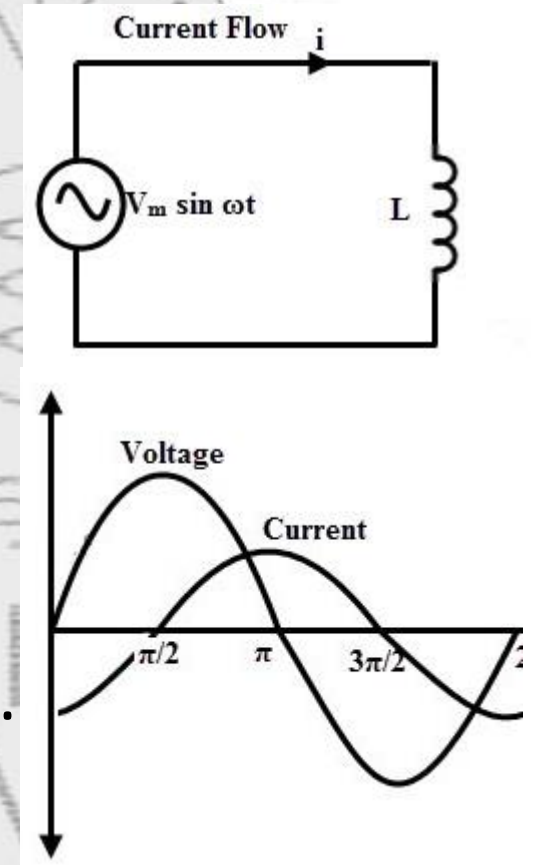


One Last Basic Electronics Concept

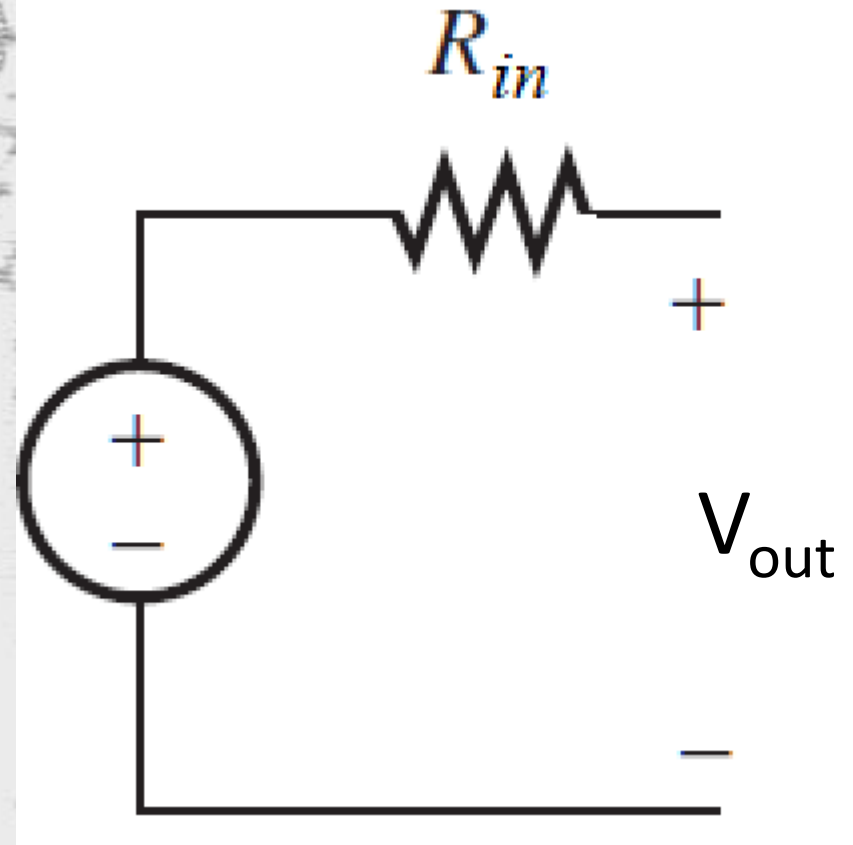- This may seem dumb but is **incredibly illustrative**.
- What is the voltage appearing at the output?
 - Zero
 - Minimum
 - Maximum
- What current exists in this circuit?
 - Zero
 - Minimum
 - Maximum




Dipole Voltage and Current Distribution

- Energy Distribution at both ends (but opposite polarity):
 - Voltage is maximum—Why? (*this is critical to understand!!!*)
 - Answer: open circuit
- Since voltage at ends is max, then voltage at the feed point (middle) must be minimum or zero.
- Therefore, what is the input impedance?
 - High (about 2k to 5k Ohms)?
 - Low (about 50 Ohms)?
 - Why your choice of answer?
 - It's all about Ohm's Law.

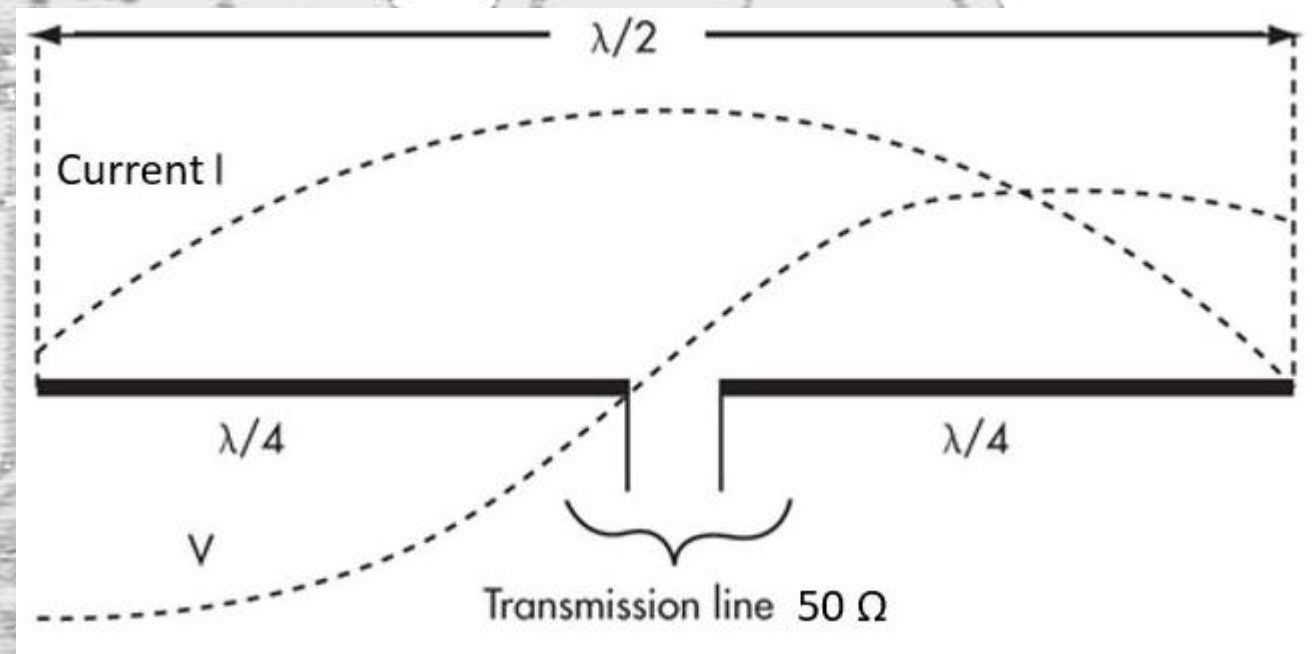



A Full Wavelength

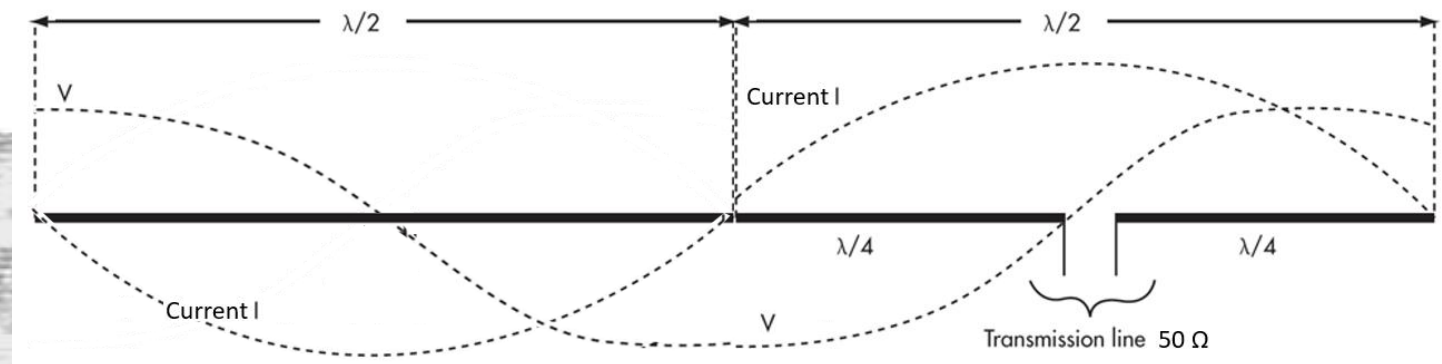- Enter a FULL WAVE dipole.
 - Feed point impedance is 50 Ohms
 - It is resonant but doesn't work.
- Why will a full wavelength dipole antenna NOT work?
- How about a $1 \frac{1}{2}$ wavelength antenna?
- Do not dismiss these as trivial concepts. They are critical if you are going to be an innovator.





Introducing the J-Pole Antenna

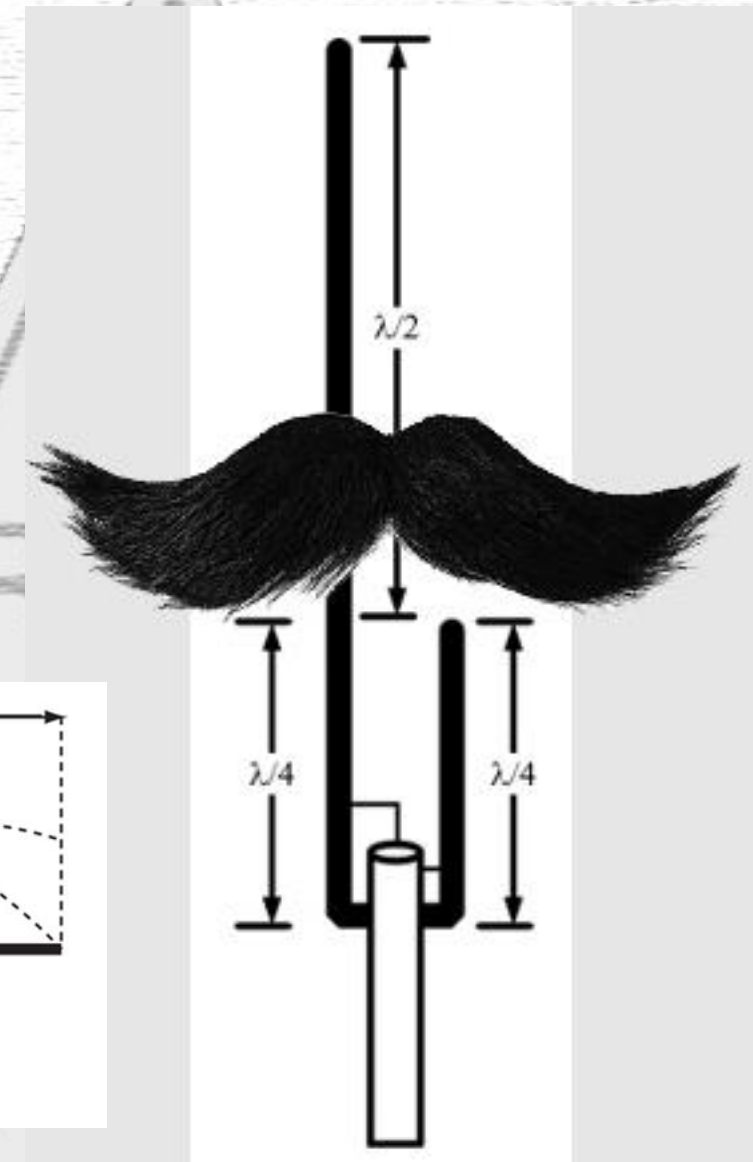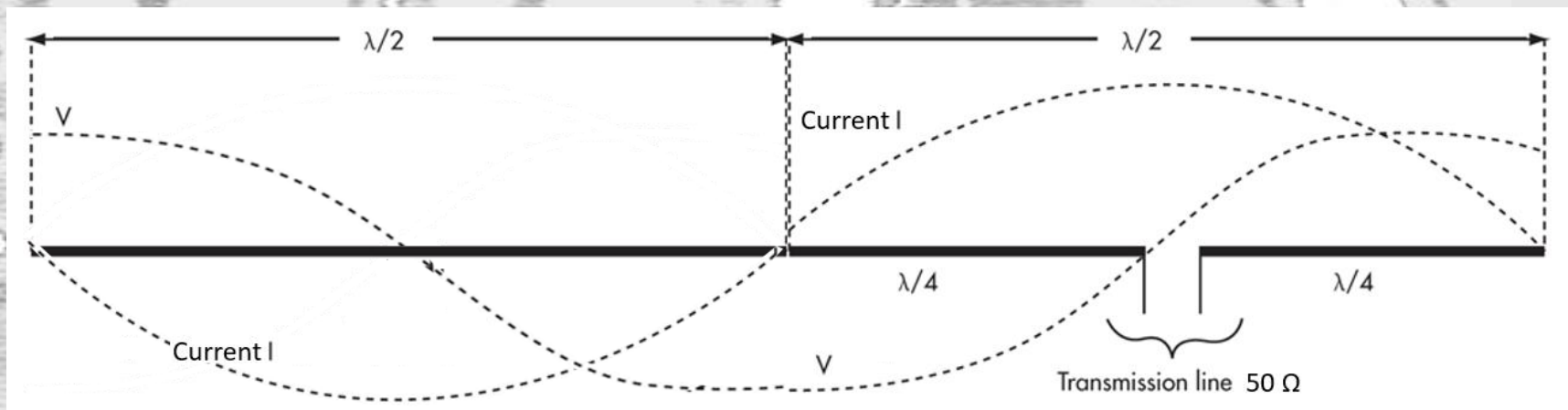- He's really a
 - full-wave di-pole antenna in disguise or
 - An end-fed half-wave di-pole in disguise.
- But full-wave di-pole's don't work!!!



Ripping Off the Disguise

- When we unfold the J-Pole...

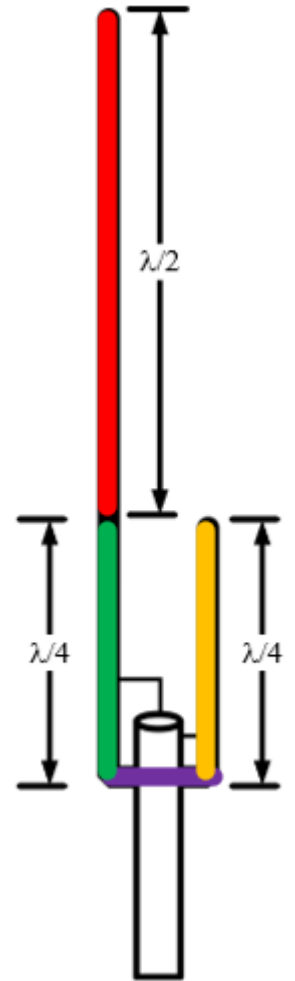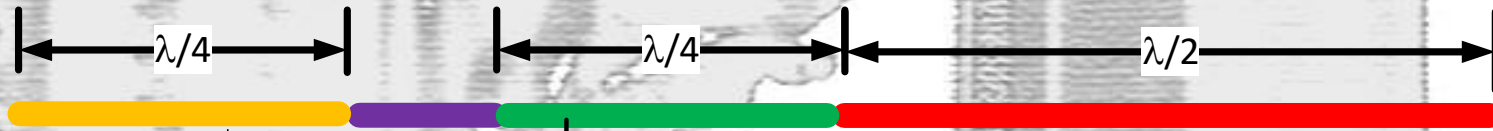

Watch an Animation...

*But wait a minute... We learned in The Mighty Dipole Part I that full-wave dipoles **don't work!** There must be an **ODD** count of half-waves. Even counts cancel themselves. But we already know from empirical results that **J-Poles** work.*



Wesley Cardone, N8QM

Questions?

